



Aswan University

**Electrical Department
First Year, 2nd Semester
Electrical Test 1**



Faculty of Engineering

**Report on
(24 hrs Digital Clock)**

Subject:

Electrical Test 3

Represented by:

Eman Mamdouh

Presented to:

Eng. Abeer

Supervised by:

Dr. Mahmoud Ali Saber

1) Draw the circuit diagram of 24 hrs digital clock.


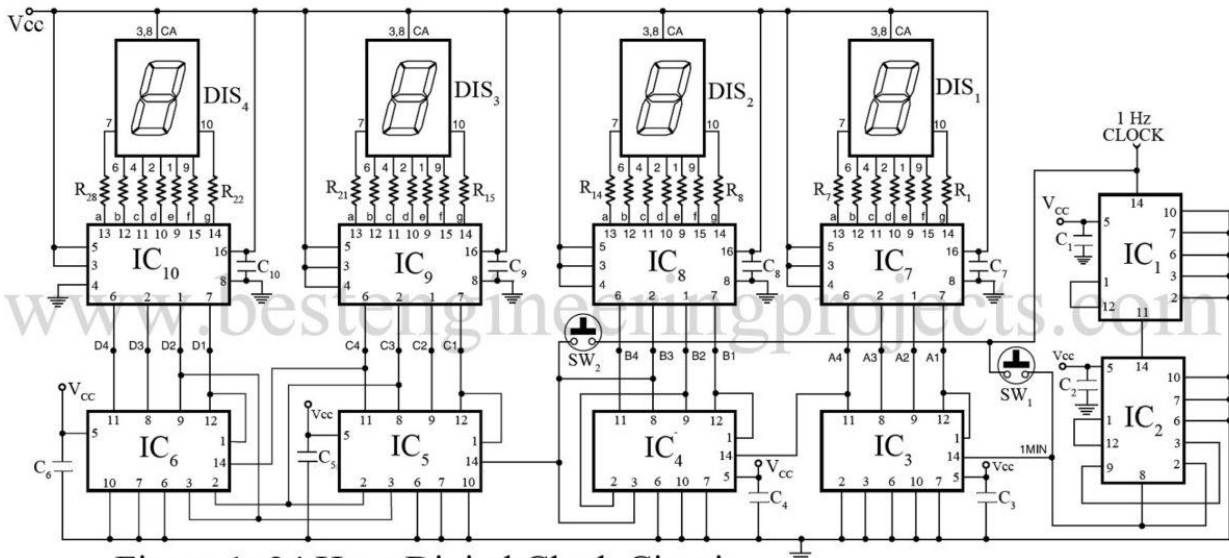


Figure 1: 24 Hour Digital Clock Circuit


2) Explain the function of each component.

- **7-segment:** to display the clock on.
- **Resistors:** to decrease the voltage entering the 7-segment in order not to damage.
- **ICs(7-10):** BCD to decimal decoders
- **IC1:** serves as divide-by-10 counter
- **IC2:** serves as divide-by-6 counter
- **IC(3,4):** serves as divide-by-60 counter (which resets at 60 min)
- **IC5:** serves as divide-by-10 counter (which resets at 4 when IC6 reaches 2)
- **IC6:** serves as divide-by-3 counter
- **Capacitors:** to decrease the noise of the signal.

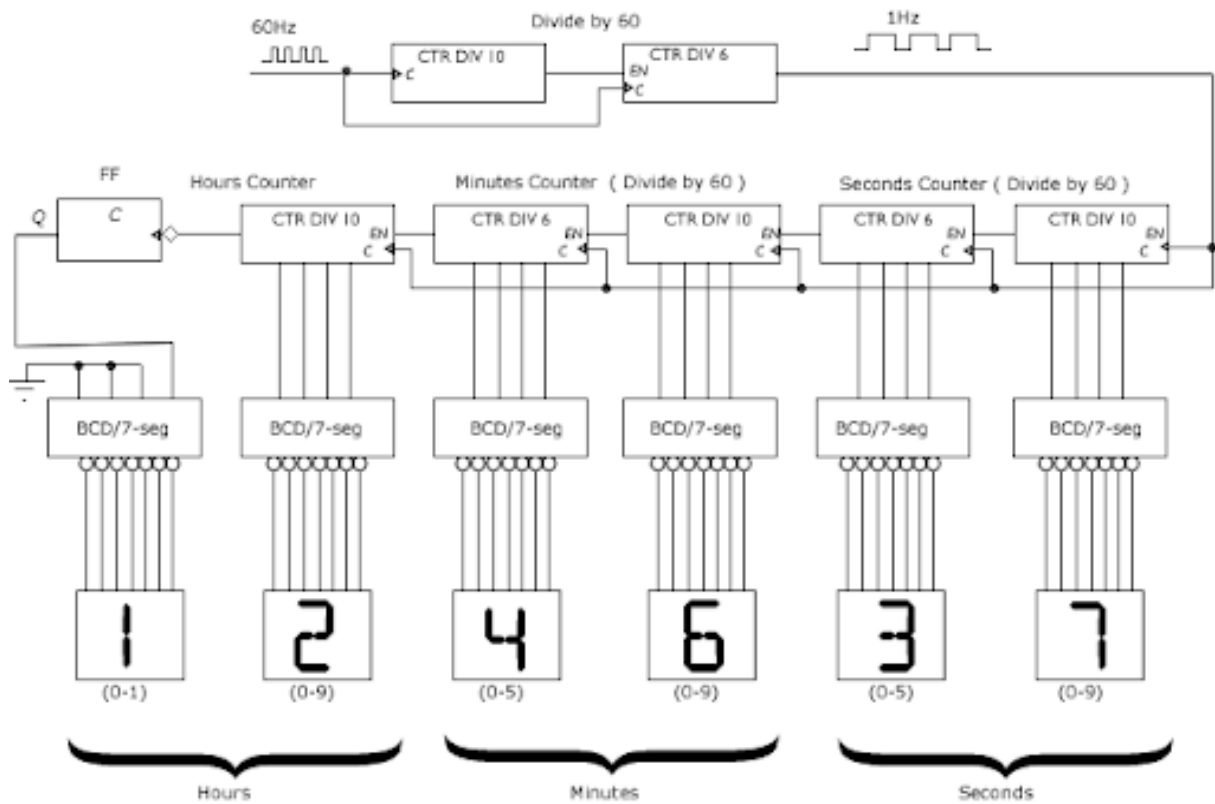
3) Extend the diagram to include seconds.



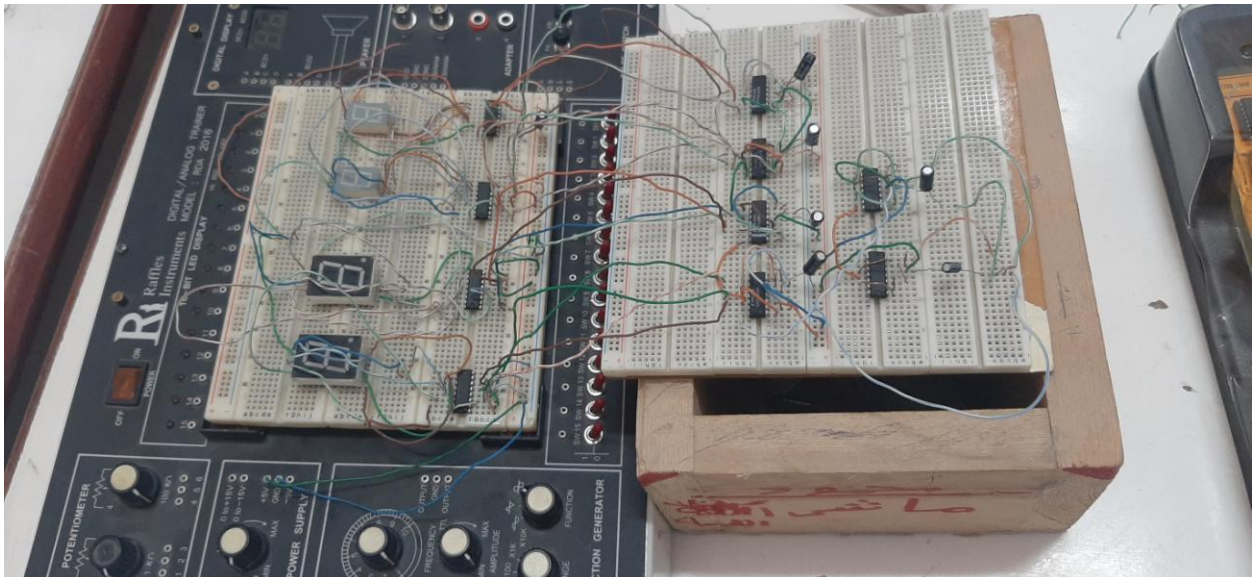4) Put a picture of your hardware connection.




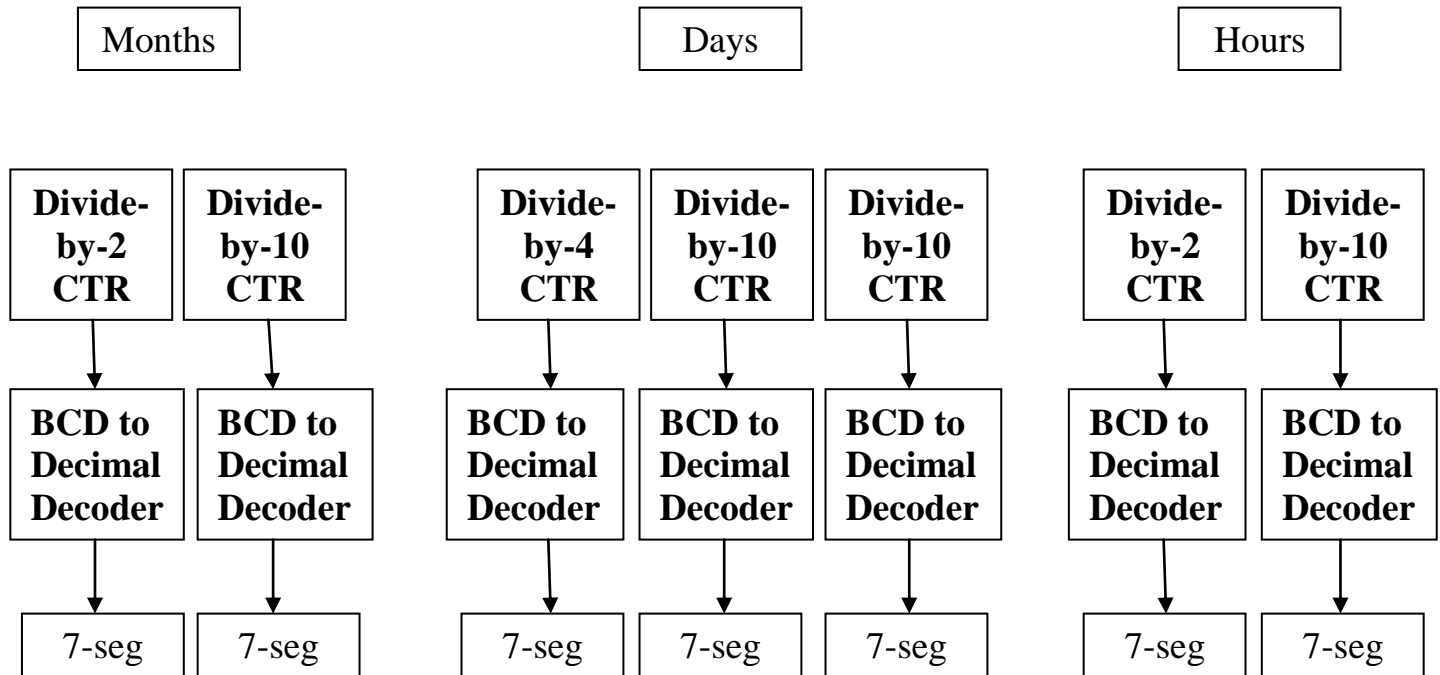5) Use divide by n counter to sketch 12hrs digital clock with months.




6) Draw the connection of counter for divide by (10-5-6-15).


Counter (divide-by-10)

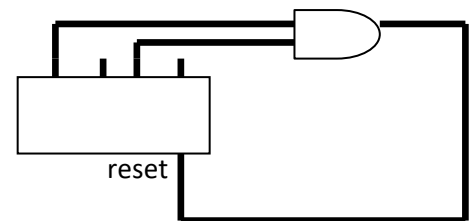

Counter (divide-by-5)

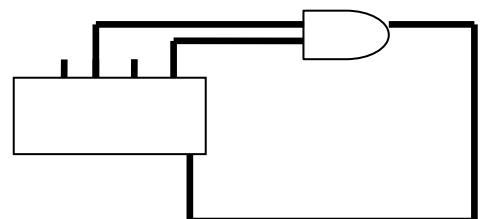

Counter (divide-by-6)

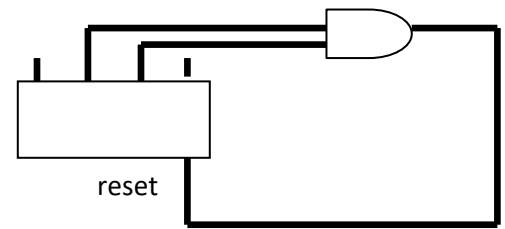

Counter (divide-by-6)

